

Which components behave differently when connecting the battery in the opposite direction?

Component	Behaves differently?	Describe the difference in behavior
Lamp		
Buzzer		
Motor		

Which components behave differently when connecting the battery in the opposite direction?

Component	Behaves differently?	Describe the difference in behavior
Lamp		
Buzzer		
Motor		

Which components behave differently when connecting the battery in the opposite direction?

Component	Behaves differently?	Describe the difference in behavior
Lamp		
Buzzer		
Motor		

